


## **CSE 30342 Lab 4 Group Submission**

Group Members: **Daniel Noronha, Ricky Ortiz, Nguyen Nguyen**

CRC Machine (Github Repo) Lab Folder: **dropbox/VLSI/boyz/lab4\_boyz**


Date: 10/29/2024
 
## Part 1&2, Problem 1 - Ring Oscillator Waveform




The initial delay is because it takes time for the ring oscillator to get an initial value at the output due to the propagation delay associated with each inverter. When the circuit is powered up initially, it takes some time for the signal to propagate through all 21 inverters and establish a stable oscillation with a fixed frequency and amplitude.
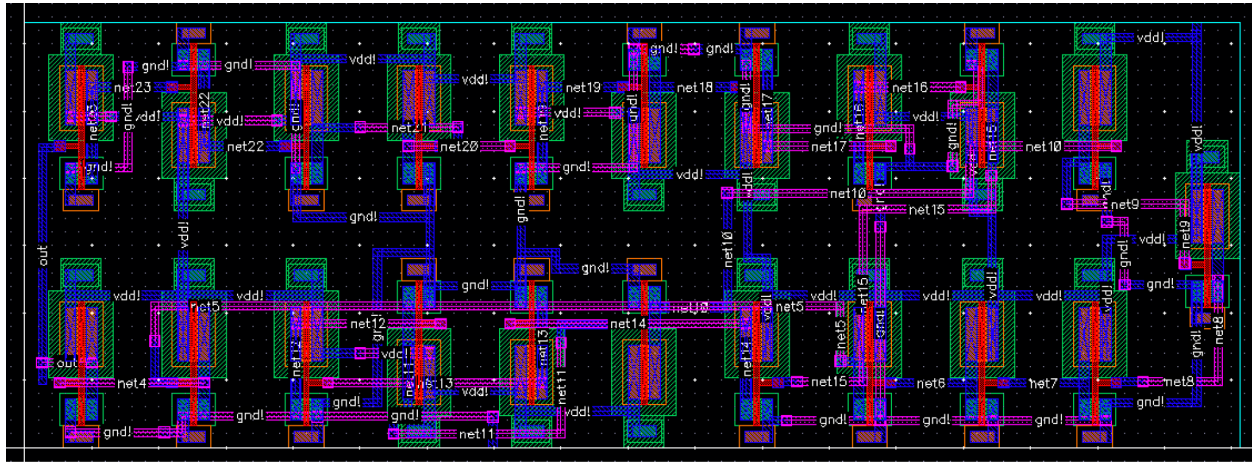
## Part 1&2, Problem 2 - Ring Oscillator Layout


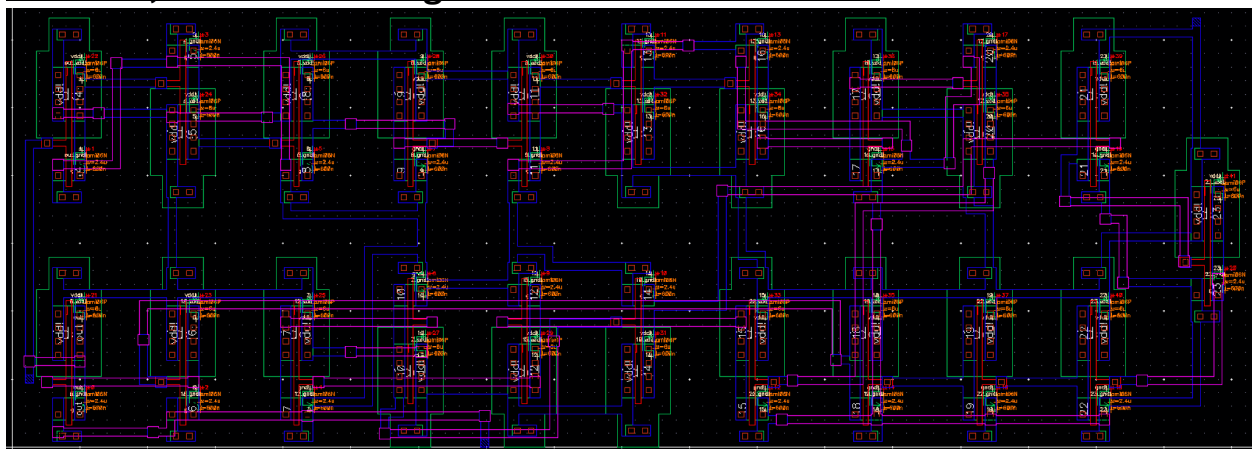
## Part 1&2, Problem 2 - Ring Oscillator Extracted View



## Part 1&2, Problem 2 - Ring Oscillator Spectre si.inp Netlist File

```
// Default Spectre Simulation run title card.  
// Generated for: spectre  
// Generated on: Oct 29 19:47:42 2024  
// Design library name: lab4_boyz_dhoronha  
// Design cell name: ring_osc  
// Design view name: schematic  
simulator lang=spectre  
global 0 vdd!  
// Included Model Files  
include "$CDK_DIR/models/spectre/standalone/ami06P.m"  
include "$CDK_DIR/models/spectre/standalone/ami06N.m"
```

```

// Library name: lab4_boyz_dnoronha
// Cell name: NMOS_IV_3
// View name: schematic
subckt NMOS_IV_3 D G S
    N0 (D G S 0) ami06N w=2.4u l=600n as=3.6e-12 ad=3.6e-12 ps=7.8u \
        pd=7.8u m=1 region=sat
ends NMOS_IV_3
// End of subcircuit definition.
// Library name: lab4_boyz_dnoronha
// Cell name: PMOS_IV_3
// View name: schematic
subckt PMOS_IV_3 D G S
    P0 (D G S vdd!) ami06P w=6u l=600n as=9e-12 ad=9e-12 ps=15.0u pd=15.0u \
        m=1 region=sat
ends PMOS_IV_3
// End of subcircuit definition.
// Library name: lab4_boyz_dnoronha
// Cell name: inv
// View name: schematic
subckt inv in out
    I1 (out in 0) NMOS_IV_3
    I0 (out in vdd!) PMOS_IV_3
ends inv
// End of subcircuit definition.
// Library name: lab4_boyz_dnoronha
// Cell name: ring_osc
// View name: schematic
I23 (out net23) inv
I24 (net23 net22) inv
I25 (net22 net21) inv
I26 (net21 net20) inv
I27 (net20 net19) inv
I28 (net19 net18) inv
I29 (net18 net17) inv
I30 (net17 net16) inv
I31 (net16 net15) inv
I32 (net15 net14) inv
I33 (net14 net13) inv

```

```

I34 (net13 net12) inv
I35 (net12 net11) inv
I36 (net11 net10) inv
I37 (net10 net9) inv
I38 (net9 net8) inv
I39 (net8 net7) inv
I40 (net7 net6) inv
I41 (net6 net5) inv
I42 (net5 net4) inv
I43 (net4 out) inv
V0 (vdd! 0) vsource type=dc dc=5
// Spectre Source Statements
// Spectre Analyses and Output Options Statements
// Output Options
simOptions options
//+   reltol = 1.00000000E-03
//+   vabstol = 1.00000000E-06
//+   iabstol = 1.00000000E-12
//+   temp = 27
//+   save = allpub
//+   currents = selected
// Analyses
// dc1 dc oppoint=logfile homotopy=all
tran1 tran start=0 stop=80n step=0.1n errpreset=moderate
// End of Netlist

```

### **Part 1&2, Problem 2 - Ring Oscillator LVS Netlist File\***

```

t 18 out output
n 1 vdd!
n 0 gnd!
n 2 /net20
n 3 /net10
n 4 /net7
n 5 /net11
n 6 /net13
n 7 /net5
n 8 /net14
n 9 /net19

```

```

n 10 /net17
n 11 /net18
n 12 /net8
n 13 /net6
n 14 /net22
n 15 /net4
n 16 /net15
n 18 /out
n 19 /net16
n 20 /net9
n 21 /net12
n 22 /net21
n 24 /net23
; nmos4 Instance /I23/I1/N0 = auLvs device Q0
d nmos D G S B (p D S)
i 0 nmos 24 18 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I23/I0/P0 = auLvs device Q1
d pmos D G S B (p D S)
i 1 pmos 24 18 1 1 " m 1 l 600e-9 w 6e-6 "
; nmos4 Instance /I24/I1/N0 = auLvs device Q2
i 2 nmos 14 24 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I24/I0/P0 = auLvs device Q3
i 3 pmos 14 24 1 1 " m 1 l 600e-9 w 6e-6 "
; nmos4 Instance /I25/I1/N0 = auLvs device Q4
i 4 nmos 22 14 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I25/I0/P0 = auLvs device Q5
i 5 pmos 22 14 1 1 " m 1 l 600e-9 w 6e-6 "
; nmos4 Instance /I26/I1/N0 = auLvs device Q6
i 6 nmos 2 22 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I26/I0/P0 = auLvs device Q7
i 7 pmos 2 22 1 1 " m 1 l 600e-9 w 6e-6 "
; nmos4 Instance /I27/I1/N0 = auLvs device Q8
i 8 nmos 9 2 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I27/I0/P0 = auLvs device Q9
i 9 pmos 9 2 1 1 " m 1 l 600e-9 w 6e-6 "
; nmos4 Instance /I28/I1/N0 = auLvs device Q10
i 10 nmos 11 9 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I28/I0/P0 = auLvs device Q11

```

i 11 pmos 11 9 1 1 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I29/I1/N0 = auLvs device Q12  
i 12 nmos 10 11 0 0 " m 1 l 600e-9 w 2.4e-6 "  
; pmos4 Instance /I29/I0/P0 = auLvs device Q13  
i 13 pmos 10 11 1 1 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I30/I1/N0 = auLvs device Q14  
i 14 nmos 19 10 0 0 " m 1 l 600e-9 w 2.4e-6 "  
; pmos4 Instance /I30/I0/P0 = auLvs device Q15  
i 15 pmos 19 10 1 1 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I31/I1/N0 = auLvs device Q16  
i 16 nmos 16 19 0 0 " m 1 l 600e-9 w 2.4e-6 "  
; pmos4 Instance /I31/I0/P0 = auLvs device Q17  
i 17 pmos 16 19 1 1 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I32/I1/N0 = auLvs device Q18  
i 18 nmos 8 16 0 0 " m 1 l 600e-9 w 2.4e-6 "  
; pmos4 Instance /I32/I0/P0 = auLvs device Q19  
i 19 pmos 8 16 1 1 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I33/I1/N0 = auLvs device Q20  
i 20 nmos 6 8 0 0 " m 1 l 600e-9 w 2.4e-6 "  
; pmos4 Instance /I33/I0/P0 = auLvs device Q21  
i 21 pmos 6 8 1 1 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I34/I1/N0 = auLvs device Q22  
i 22 nmos 21 6 0 0 " m 1 l 600e-9 w 2.4e-6 "  
; pmos4 Instance /I34/I0/P0 = auLvs device Q23  
i 23 pmos 21 6 1 1 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I35/I1/N0 = auLvs device Q24  
i 24 nmos 5 21 0 0 " m 1 l 600e-9 w 2.4e-6 "  
; pmos4 Instance /I35/I0/P0 = auLvs device Q25  
i 25 pmos 5 21 1 1 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I36/I1/N0 = auLvs device Q26  
i 26 nmos 3 5 0 0 " m 1 l 600e-9 w 2.4e-6 "  
; pmos4 Instance /I36/I0/P0 = auLvs device Q27  
i 27 pmos 3 5 1 1 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I37/I1/N0 = auLvs device Q28  
i 28 nmos 20 3 0 0 " m 1 l 600e-9 w 2.4e-6 "  
; pmos4 Instance /I37/I0/P0 = auLvs device Q29  
i 29 pmos 20 3 1 1 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I38/I1/N0 = auLvs device Q30

```

i 30 nmos 12 20 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I38/I0/P0 = auLvs device Q31
i 31 pmos 12 20 1 1 " m 1 l 600e-9 w 6e-6 "
; nmos4 Instance /I39/I1/N0 = auLvs device Q32
i 32 nmos 4 12 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I39/I0/P0 = auLvs device Q33
i 33 pmos 4 12 1 1 " m 1 l 600e-9 w 6e-6 "
; nmos4 Instance /I40/I1/N0 = auLvs device Q34
i 34 nmos 13 4 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I40/I0/P0 = auLvs device Q35
i 35 pmos 13 4 1 1 " m 1 l 600e-9 w 6e-6 "
; nmos4 Instance /I41/I1/N0 = auLvs device Q36
i 36 nmos 7 13 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I41/I0/P0 = auLvs device Q37
i 37 pmos 7 13 1 1 " m 1 l 600e-9 w 6e-6 "
; nmos4 Instance /I42/I1/N0 = auLvs device Q38
i 38 nmos 15 7 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I42/I0/P0 = auLvs device Q39
i 39 pmos 15 7 1 1 " m 1 l 600e-9 w 6e-6 "
; nmos4 Instance /I43/I1/N0 = auLvs device Q40
i 40 nmos 18 15 0 0 " m 1 l 600e-9 w 2.4e-6 "
; pmos4 Instance /I43/I0/P0 = auLvs device Q41
i 41 pmos 18 15 1 1 " m 1 l 600e-9 w 6e-6 "
t 0 gnd! global
t 1 vdd! global


```

**\*Both LVS and Spectre (si.inp) netlist files were included because directions were not specific (asked for si.inp from LVS.ring\_osc folder but si.inp only exists in Spectre run directory).**





### Part 3, Problem 3 - Layout

 


This figure shows a detailed layout of a 16-bit 1T1R1C1 array. The layout includes various components such as SumNeg, CoutNeg, and various capacitors and resistors. The layout is color-coded, with different colors representing different types of components or layers. The layout is organized into a grid, with the array elements arranged in rows and columns. The layout also includes peripheral logic, such as input and output buffers, and a clock distribution network. The layout is labeled with various parameters, such as dimensions, capacitance, and resistance, which are used to define the physical properties of the components. The layout is a complex design, and it is important to understand the various components and their connections in order to fabricate the device correctly.


### Part 3, Problem 3 - Mirror Full Adder LVS Netlist File

```
i 13 nmos 11 18 6 0 " m 1 l 600e-9 w 1.5e-6 "  
; nmos4 Instance /I18/N0 = auLvs device Q14  
i 14 nmos 4 2 11 0 " m 1 l 600e-9 w 1.5e-6 "  
; nmos4 Instance /I17/N0 = auLvs device Q15  
i 15 nmos 15 3 0 0 " m 1 l 600e-9 w 1.5e-6 "  
; nmos4 Instance /I16/N0 = auLvs device Q16  
i 16 nmos 15 18 0 0 " m 1 l 600e-9 w 1.5e-6 "  
; nmos4 Instance /I15/N0 = auLvs device Q17  
i 17 nmos 15 2 0 0 " m 1 l 600e-9 w 1.5e-6 "  
; nmos4 Instance /I14/N0 = auLvs device Q18  
i 18 nmos 14 18 0 0 " m 1 l 600e-9 w 1.5e-6 "  
; nmos4 Instance /I13/N0 = auLvs device Q19  
i 19 nmos 4 5 15 0 " m 1 l 600e-9 w 1.5e-6 "  
; nmos4 Instance /I12/N0 = auLvs device Q20  
i 20 nmos 5 2 14 0 " m 1 l 600e-9 w 1.5e-6 "  
; nmos4 Instance /I23/N0 = auLvs device Q21  
i 21 nmos 9 2 0 0 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I22/N0 = auLvs device Q22  
i 22 nmos 9 18 0 0 " m 1 l 600e-9 w 6e-6 "  
; nmos4 Instance /I21/N0 = auLvs device Q23  
i 23 nmos 5 3 9 0 " m 1 l 600e-9 w 6e-6 "  
t 0 gnd! global  
t 1 vdd! global
```

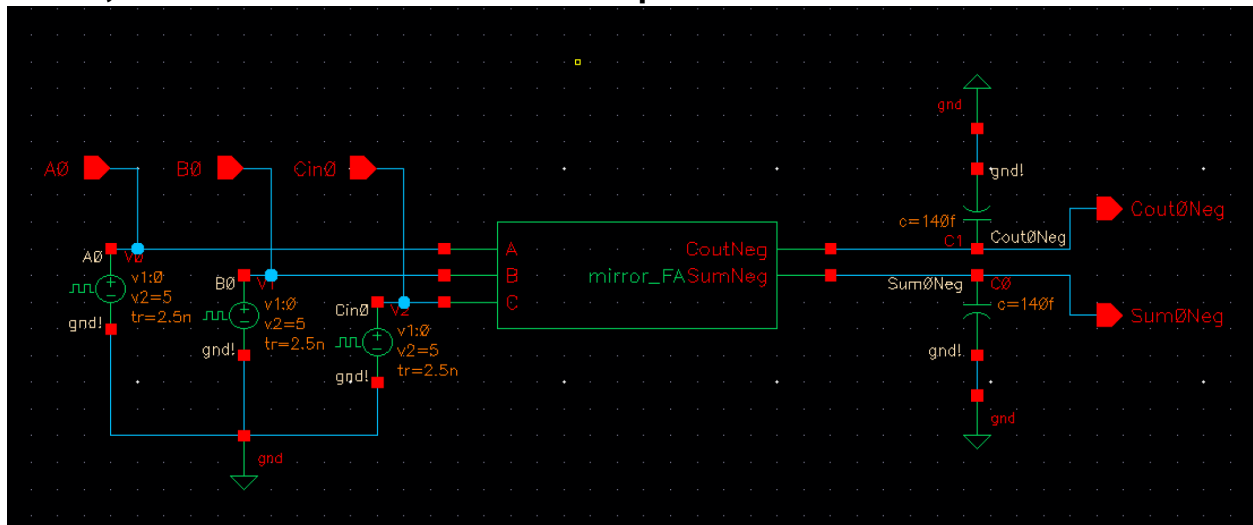
### Part 3, Problem 4 - Mirror Full Adder Spectre Schematic


 
## Part 3, Problem 4 - Mirror Full Adder Spectre Waveform (Cout0Neg)


 
## Part 3, Problem 4 - Mirror Full Adder Spectre Waveform (Sum0Neg)



### **Part 3, Problem 4 - Mirror Full Adder Spectre si.inp Netlist File**

```
// Default Spectre Simulation run title card.
// Generated for: spectre
// Generated on: Oct 29 23:46:35 2024
// Design library name: lab4_boyz_nnguye24
// Design cell name: sim_mirror_FA
// Design view name: schematic
simulator lang=spectre
global 0 vdd!
// Included Model Files
include "$CDK_DIR/models/spectre/standalone/ami06P.m"
include "$CDK_DIR/models/spectre/standalone/ami06N.m"
// Library name: lab4_boyz_nnguye24
// Cell name: pmos_8l
// View name: schematic
subckt pmos_8l D G S
    P0 (D G S vdd!) ami06P w=12.0u l=600n as=1.8e-11 ad=1.8e-11 ps=27.0u \
        pd=27.0u m=1 region=sat
ends pmos_8l
// End of subcircuit definition.
// Library name: lab4_boyz_nnguye24
// Cell name: pmos_1l
// View name: schematic
subckt pmos_1l D G S
    P0 (D G S vdd!) ami06P w=1.5u l=600n as=2.25e-12 ad=2.25e-12 ps=6u \
        pd=6u m=1 region=sat
ends pmos_1l
// End of subcircuit definition.
// Library name: lab4_boyz_nnguye24
// Cell name: nmos_1l
// View name: schematic
subckt nmos_1l D G S
    N0 (D G S 0) ami06N w=1.5u l=600n as=2.25e-12 ad=2.25e-12 ps=6u pd=6u \
        m=1 region=sat
ends nmos_1l
// End of subcircuit definition.
// Library name: lab4_boyz_nnguye24
// Cell name: nmos_4l
// View name: schematic
subckt nmos_4l D G S
    N0 (D G S 0) ami06N w=6u l=600n as=9e-12 ad=9e-12 ps=15.0u pd=15.0u \
        m=1 region=sat
ends nmos_4l
// End of subcircuit definition.
```

```

// Library name: lab4_boyz_nnguye24
// Cell name: mirror_FA
// View name: schematic
subckt mirror_FA A B C CoutNeg SumNeg
  I2 (CoutNeg C net32) pmos_8l
  I1 (net32 B vdd!) pmos_8l
  I0 (net32 A vdd!) pmos_8l
  I11 (SumNeg A net54) pmos_1l
  I10 (net54 B net55) pmos_1l
  I9 (net55 C vdd!) pmos_1l
  I8 (net41 C vdd!) pmos_1l
  I7 (net41 B vdd!) pmos_1l
  I6 (SumNeg CoutNeg net41) pmos_1l
  I5 (net41 A vdd!) pmos_1l
  I4 (CoutNeg A net51) pmos_1l
  I3 (net51 B vdd!) pmos_1l
  I20 (net48 C 0) nmos_1l
  I19 (net49 B net48) nmos_1l
  I18 (SumNeg A net49) nmos_1l
  I17 (net40 C 0) nmos_1l
  I16 (net40 B 0) nmos_1l
  I15 (net40 A 0) nmos_1l
  I14 (net50 B 0) nmos_1l
  I13 (SumNeg CoutNeg net40) nmos_1l
  I12 (CoutNeg A net50) nmos_1l
  I23 (net30 A 0) nmos_4l
  I22 (net30 B 0) nmos_4l
  I21 (CoutNeg C net30) nmos_4l
  V0 (vdd! 0) vsource type=dc dc=5
ends mirror_FA
// End of subcircuit definition.
// Library name: lab4_boyz_nnguye24
// Cell name: sim_mirror_FA
// View name: schematic
I0 (A0 B0 Cin0 Cout0Neg Sum0Neg) mirror_FA
V2 (Cin0 0) vsource type=pulse val0=0 val1=5 period=4u delay=10n rise=2.5n \
  fall=2.5n width=1.9975u
V1 (B0 0) vsource type=pulse val0=0 val1=5 period=2u delay=10n rise=2.5n \
  fall=2.5n width=997.5n
V0 (A0 0) vsource type=pulse val0=0 val1=5 period=1u delay=10n rise=2.5n \
  fall=2.5n width=497.5n
C1 (Cout0Neg 0) capacitor c=140f m=1
C0 (Sum0Neg 0) capacitor c=140f m=1
// Spectre Source Statements

```

```
// Spectre Analyses and Output Options Statements
// Output Options
simOptions options
//+   reltol = 1.00000000E-03
//+   vabstol = 1.00000000E-06
//+   iabstol = 1.00000000E-12
//+   temp = 27
//+   save = allpub
//+   currents = selected
// Analyses
// dc1 dc oppoint=logfile homotopy=all
tran1 tran start=0 stop=4.1u step=0.1n errpreset=moderate
// End of Netlist
```